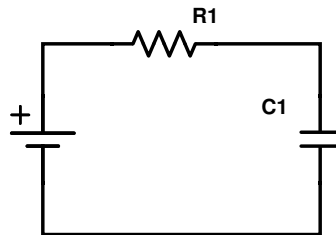


## RC TRANSIENTS IN-BRIEF

RC circuits exhibit transient time-dependent behaviour. Below two cases are shown in brief: charging when first connected to a voltage source (e.g. battery), and discharging when first shorted across a resistor. The Kirchhoff's law equation is used to establish a differential equation describing the charging behaviour and from there  $q(t)$ ,  $I(t)$  and  $V_C(t)$  can be determined.

**charging**




Kirchoff's law:  $V_B - IR_1 - V_C = 0; I = \frac{dq}{dt}$

Rearranging:  $V_B - \frac{dq}{dt}R_1 - \frac{q}{C_1}$

1st order DE:  $\frac{dq}{dt} = \frac{1}{R_1}(V_B - \frac{q}{C_1})$

solving for  $q(t)$ :  $q(t) = C_1V_B(1 - e^{-t/R_1C_1})$


$$C_1V_B = Q_{max}$$

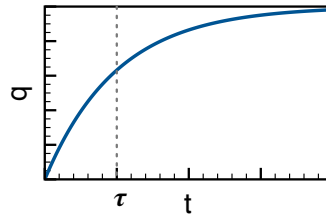

solving for  $V_C(t) = q/C_1$ :  $V_C(t) = V_B(1 - e^{-t/R_1C_1})$

solving for  $I(t) = \frac{dq}{dt}$ :  $I(t) = I_0e^{-t/R_1C_1}$

**discharging**

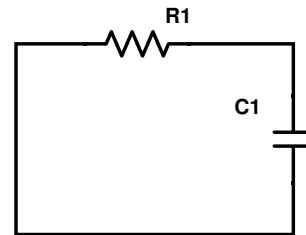


$V_C - IR_1 = 0; I = -\frac{dq}{dt}$

$\frac{q}{C_1} + \frac{dq}{dt}R_1 = 0$

$\frac{dq}{dt} = -\frac{q}{R_1C_1}$

$q(t) = Q_0e^{-t/R_1C_1}$

$Q_0 = \text{initial charge}$

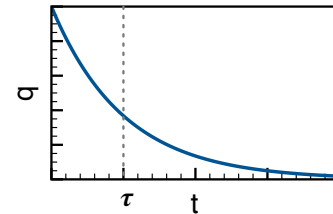

$V_C(t) = V_0e^{-t/R_1C_1}$

$I(t) = I_0e^{-t/R_1C_1}$

Typically we define a "time constant"  $\tau = RC$  which is a characteristic decay time of the exponential (like in other decaying systems), such that the exponentials become  $e^{-t/\tau}$ .  $\tau$  is the time it takes for a decaying exponential to reach  $1/e$  of its initial value, and can be read directly off a graph.